

## CA\_Lab1

K. Ram Mohan

COE19B055

### Verilog Code:

```
// Module to compare exponent values of inputs
```

```
module CMP_EXP(ea, eb, sign_var);
```

```
    input[10:0] ea, eb;
```

```
    output reg[1:0] sign_var;
```

```
    always @(*) begin
```

```
        if (ea>eb) begin
```

```
            sign_var = 2'b00;
```

```
        end
```

```
        if (ea<eb) begin
```

```
            sign_var = 2'b01;
```

```
        end
```

```
        if(ea==eb) begin
```

```
            sign_var = 2'b10;
```

```
        end
```

```
    end
```

```
endmodule
```

```
// Module to swap inputs if necessary
```

```

module SWAP_M (ma, mb, sa, sb, ea, eb, sign_var, outa, outb, sa_out, sb_out, ea_out,
eb_out);

    input[52:0] ma, mb;
    input[1:0] sign_var;
    input sa, sb;
    input[10:0] ea, eb;

    output reg[52:0] outa, outb;
    output reg sa_out, sb_out;
    output reg[10:0] ea_out, eb_out;

    always @(*) begin
        if (sign_var==2'b00) begin
            outa = ma;
            outb = mb;
            sa_out = sa;
            sb_out = sb;
            ea_out = ea;
            eb_out = eb;
        end

        if (sign_var==2'b01) begin
            outa = mb;
            outb = ma;
            sa_out = sb;
            sb_out = sa;
            ea_out = eb;
            eb_out = ea;
        end
    end
end

```

```

if (sign_var==2'b10) begin
    if(ma>=mb) begin
        outa = ma;
        outb = mb;
        sa_out = sa;
        sb_out = sb;
        ea_out = ea;
        eb_out = eb;
    end

    if(ma < mb) begin
        outa = mb;
        outb = ma;
        sa_out = sb;
        sb_out = sa;
        ea_out = eb;
        eb_out = ea;
    end
end
end
endmodule

// Module to find difference of exponents
module DIFF_EXP (ea, eb, out);
    input[10:0] ea, eb;
    output reg[10:0] out;

    always @(*) begin
        if (ea>=eb) begin

```

```

        out = ea-eb;
    end

    if (ea<eb) begin
        out = eb-ea;
    end
end
endmodule

// Module to shift smaller value
module RHT_SFT (mb, len, out);
    input[52:0] mb;
    input[10:0] len;
    output[52:0] out;

    assign out = mb >> len;
endmodule

// Module for Full adder
module FA (in0, in1, cin, sum, cout);
    input in0, in1, cin;
    output sum, cout;

    wire c1, c2, c3;

    xor(sum, in0, in1, cin);
    and(c1, in0, in1);
    xor(c2, in0, in1);
    and(c3, c2, cin);

```

```
    or(cout, c1, c3);  
endmodule
```

```
// Module to add same sign variables
```

```
module SAME_SIGN_ADD (ma, mb, out, cout);
```

```
    input[52:0] ma, mb;
```

```
    output[52:0] out;
```

```
    output cout;
```

```
    wire[52:0] sum;
```

```
    wire[52:0] tmp;
```

```
    FA fa1(ma[0], mb[0], 1'b0, sum[0], tmp[0]);
```

```
    FA fa2(ma[1], mb[1], tmp[0], sum[1], tmp[1]);
```

```
    FA fa3(ma[2], mb[2], tmp[1], sum[2], tmp[2]);
```

```
    FA fa4(ma[3], mb[3], tmp[2], sum[3], tmp[3]);
```

```
    FA fa5(ma[4], mb[4], tmp[3], sum[4], tmp[4]);
```

```
    FA fa6(ma[5], mb[5], tmp[4], sum[5], tmp[5]);
```

```
    FA fa7(ma[6], mb[6], tmp[5], sum[6], tmp[6]);
```

```
    FA fa8(ma[7], mb[7], tmp[6], sum[7], tmp[7]);
```

```
    FA fa9(ma[8], mb[8], tmp[7], sum[8], tmp[8]);
```

```
    FA fa10(ma[9], mb[9], tmp[8], sum[9], tmp[9]);
```

```
    FA fa11(ma[10], mb[10], tmp[9], sum[10], tmp[10]);
```

```
    FA fa12(ma[11], mb[11], tmp[10], sum[11], tmp[11]);
```

```
    FA fa13(ma[12], mb[12], tmp[11], sum[12], tmp[12]);
```

```
    FA fa14(ma[13], mb[13], tmp[12], sum[13], tmp[13]);
```

FA fa15(ma[14], mb[14], tmp[13], sum[14], tmp[14]);  
FA fa16(ma[15], mb[15], tmp[14], sum[15], tmp[15]);  
FA fa17(ma[16], mb[16], tmp[15], sum[16], tmp[16]);  
FA fa18(ma[17], mb[17], tmp[16], sum[17], tmp[17]);  
FA fa19(ma[18], mb[18], tmp[17], sum[18], tmp[18]);

FA fa20(ma[19], mb[19], tmp[19], sum[19], tmp[19]);  
FA fa21(ma[20], mb[20], tmp[17], sum[20], tmp[20]);  
FA fa22(ma[21], mb[21], tmp[20], sum[21], tmp[21]);  
FA fa23(ma[22], mb[22], tmp[21], sum[22], tmp[22]);  
FA fa24(ma[23], mb[23], tmp[22], sum[23], tmp[23]);  
FA fa25(ma[24], mb[24], tmp[23], sum[24], tmp[24]);

FA fa26(ma[25], mb[25], tmp[24], sum[25], tmp[25]);  
FA fa27(ma[26], mb[26], tmp[25], sum[26], tmp[26]);  
FA fa28(ma[27], mb[27], tmp[26], sum[27], tmp[27]);  
FA fa29(ma[28], mb[28], tmp[27], sum[28], tmp[28]);  
FA fa30(ma[29], mb[29], tmp[28], sum[29], tmp[29]);  
FA fa31(ma[30], mb[30], tmp[29], sum[30], tmp[30]);

FA fa32(ma[31], mb[31], tmp[30], sum[31], tmp[31]);  
FA fa33(ma[32], mb[32], tmp[31], sum[32], tmp[32]);  
FA fa34(ma[33], mb[33], tmp[32], sum[33], tmp[33]);  
FA fa35(ma[34], mb[34], tmp[33], sum[34], tmp[34]);

```
FA fa36(ma[35], mb[35], tmp[34], sum[35], tmp[35]);
```

```
FA fa37(ma[36], mb[36], tmp[35], sum[36], tmp[36]);
```

```
FA fa38(ma[37], mb[37], tmp[36], sum[37], tmp[37]);
```

```
FA fa39(ma[38], mb[38], tmp[37], sum[38], tmp[38]);
```

```
FA fa40(ma[39], mb[39], tmp[38], sum[39], tmp[39]);
```

```
FA fa41(ma[40], mb[40], tmp[39], sum[40], tmp[40]);
```

```
FA fa42(ma[41], mb[41], tmp[40], sum[41], tmp[41]);
```

```
FA fa43(ma[42], mb[42], tmp[41], sum[42], tmp[42]);
```

```
FA fa44(ma[43], mb[43], tmp[42], sum[43], tmp[43]);
```

```
FA fa45(ma[44], mb[44], tmp[43], sum[44], tmp[44]);
```

```
FA fa46(ma[45], mb[45], tmp[44], sum[45], tmp[45]);
```

```
FA fa47(ma[46], mb[46], tmp[45], sum[46], tmp[46]);
```

```
FA fa48(ma[47], mb[47], tmp[46], sum[47], tmp[47]);
```

```
FA fa49(ma[48], mb[48], tmp[47], sum[48], tmp[48]);
```

```
FA fa50(ma[49], mb[49], tmp[48], sum[49], tmp[49]);
```

```
FA fa51(ma[50], mb[50], tmp[49], sum[50], tmp[50]);
```

```
FA fa52(ma[51], mb[51], tmp[50], sum[51], tmp[51]);
```

```
FA fa53(ma[52], mb[52], tmp[51], sum[52], cout);
```

```
// FA fa54(ma[53], mb[53], tmp[52], sum[53], tmp[53]);
```

```
assign out = sum;
```

```
endmodule
```

```

// Module to add mantissas
module SUM_MANT (sa, sb, ma, mb, out, carry);

    input sa, sb;
    input[52:0] ma, mb;

    output reg carry;
    // output carry;

    wire[52:0] sum;
    wire carry1;
    output reg [52:0] out;
    // output[52:0] out;

    reg[52:0] tmp1, tmp2, tmp_sum;
    reg[52:0] tmp;

    always @(*) begin
        if(sa==sb) begin
            // tmp1 = {1'b0, ma};
            // tmp2 = {1'b0, mb};

            tmp1 = ma;
            tmp2 = mb;
        end

        if(sa==1'b1 & sb==1'b0) begin
            tmp = ~mb+1;

```



```

    // tmp1 = {1'b0, ma};
    // tmp2 = {1'b0, tmp};
    tmp1 = ma;
    tmp2 = tmp;
end

if(sa==1'b0 & sb==1'b1) begin
    tmp = ~mb+1;
    // tmp1 = {1'b0, ma};
    // tmp2 = {1'b0, tmp};
    tmp1 = ma;
    tmp2 = tmp;
end
end

SAME_SIGN_ADD same_sign_add1(tmp1, tmp2, sum, carry1);

always @(*) begin
    if(sa==sb) begin
        carry = carry1;
        out = sum;
    end

    if((sa==1 & sb==0)|(sa==0 & sb==1))begin
        if(carry1==1'b0) begin
            carry = 0;
            tmp = ~sum+1;
            // tmp = 52'b0;
            out = tmp;
        end
    end
end

```

```

        // out = ~sum[52:0]+1;
    end

    if(carry1==1'b1)begin
        carry = 0;
        out = sum;
    end
end
end

// assign out = sum;
// assign carry = carry1;
endmodule

// Module to normalize the result
module NORM_RES (sum1, carry, er, sr, mr, er_new);
    input[52:0] sum1;
    input carry, sr;
    input[10:0] er;
    output reg[51:0] mr;
    output reg[10:0] er_new;

    reg[52:0] tmp;

    always @(sum1) begin
        if(carry==1) begin
            tmp = sum1 >> 1;
            tmp[52] = carry;
            er_new = er + 1;
        end
    end
endmodule

```

```

        mr = tmp[51:0];
    end
    else begin
        if(sum1[52]==1) begin
            mr = sum1[51:0];
            er_new = er;
        end
        else begin
            tmp = sum1;
            er_new = er;
            while(tmp[52]!=1'b1) begin
                tmp = tmp << 1;
                er_new = er_new - 1;
            end

            mr = tmp[51:0];
        end
    end
end
end
endmodule

```

// Main module

```

module FP_ADDER(a, b, out);
    input[63:0] a, b;
    output[63:0] out;

    wire[1:0] sign_var;
    wire max;

```

```
wire[63:0] new_a, new_b;    // Variable for new inputs that r used after swapping small  
one to b
```

```
wire sa, sb;                // Variables for storing signs of original inputs
```

```
wire[10:0] ea, eb;          // Variables for storing expo of original inputs
```

```
wire[52:0] ma, mb;          // Variables for storing mantissa of original inputs
```

```
// Declaring output individul variables
```

```
wire sr;
```

```
wire[10:0] er;
```

```
wire[51:0] mr;
```

```
wire[52:0] sum_mantissa;
```

```
wire carry;
```

```
wire[10:0] er_new;
```

```
wire[10:0] diff_exp;        // Variable to store difference of exponents
```

```
wire[52:0] ma_new, mb_new, mb_sft;
```

```
wire sa_new, sb_new;
```

```
wire[10:0] ea_new, eb_new;
```

```
// Assigning the components to inputs to individual variables. Added one before mantissa  
that is 1 before decimal
```

```
assign sa = a[63];
```

```
assign ea = a[62: 52];
```

```
assign ma = {1'b1,a[51:0]};
```

```
assign sb = b[63];
```

```
assign eb = b[62: 52];
```

```
assign mb = {1'b1,b[51:0]};
```

```

// Finding the max value among inputs
CMP_EXP cmp_exp1(ea, eb, sign_var);

// Swapping the inputs(if necessary) such that min is in b
SWAP_M swap_m1(ma, mb, sa, sb, ea, eb, sign_var, ma_new, mb_new, sa_new, sb_new,
ea_new, eb_new);

// Finding difference of exponents
DIFF_EXP diff_exp1(ea, eb, diff_exp);

// Shifting the smaller mantissa based on difference of exponents
RHT_SFT rht_sft1(mb_new, diff_exp, mb_sft);

// Assigning sign and exponent to results
assign er = ea_new;
assign sr = sa_new;

// Adding the two mantissa
SUM_MANT sum_mant1(sa_new, sb_new, ma_new, mb_sft, sum_mantissa, carry);
// Here sum_mantissa contains 53 bits including the explicit 1 before the decimal

// Normalizing the result
NORM_RES norm_res1(sum_mantissa, carry, er, sr, mr, er_new);

assign out = {sr, er_new, mr};
endmodule

```

[illegible]

```
// a=-5.0005(approx) b=0.5005(approax)

// sum = -4.5(approx)

// 1100000000000010000000000000000000000000000010000000000000000000
#10
a=64'b110000000000101000000000001000001100010010011011101001011110001101;
b=64'b001111111111000000000001000001100010010011011101001011110001101010;

end


initial begin

    $monitor("a=%b b=%b sum=%b", a, b, out);

end


endmodule
```

### Output:

Test cases:

1.  $a=1; b=-3$
2.  $a=1; b=1.0000000000000002$
3.  $a=1.5; b=-3$
4.  $a=5.0004999999999972288833305356$ (approx.)  
 $b=1.5004999999999994493293797859$ (approx.)
5.  $a=-5.0005$ (approx.)  $b=0.5005$ (approx.)

```
C:\Users\rammo\OneDrive\Documents\CA\Lab\Lab1>iverilog -o fp fp_add
er.v

C:\Users\rammo\OneDrive\Documents\CA\Lab\Lab1>vvp fp
a=0011111111111000000000000000000000000000000000000000000000000000
b=1100000000001000000000000000000000000000000000000000000000000000
sum=1100000000000000000000000000000000000000000000000000000000000000
0
a=0011111111111000000000000000000000000000000000000000000000000000
b=0011111111111000000000000000000000000000000000000000000000000001
sum=0100000000000100000000000000000000000000000000000000000000000000
0
a=0011111111111000000000000000000000000000000000000000000000000000
b=1100000000001000000000000000000000000000000000000000000000000000
sum=1011111111111000000000000000000000000000000000000000000000000000
0
a=110000000000101000000000001000001100010010011011101001011110001101
b=00111111111110000000000100000110001001001101110100101111000110101
sum=1100000000001100000000000000000000000000000000100000000000000000
0
a=110000000000101000000000001000001100010010011011101001011110001101
b=001111111111000000000001000001100010010011011101001011110001101010
sum=1100000000001001000000000000000000000000000000010000000000000000
0
C:\Users\rammo\OneDrive\Documents\CA\Lab\Lab1>
```